



الأكاديمية العربية للعلوم والتكنولوجيا والنقل البحري

Arab Academy for Science, Technology & Maritime Transport

MIPS

Name: Mahmoud Mostafa Mahmoud Ramadan

Reg No.: 19102461

Dr. Ahmed Abo El Farag

Eng. Esraa Khattab



Sources Needed for Mips

1) Program Counter

VHDL Module:

```
33 entity PCounter is
34     Port ( Pc_In : in  STD_LOGIC_VECTOR (31 downto 0);
35           CLK : in  STD_LOGIC;
36           Pc_Out : out  STD_LOGIC_VECTOR (31 downto 0));
37 end PCounter;
38
39 architecture Behavioral of PCounter is
40     signal temp : STD_LOGIC_VECTOR (31 downto 0) := X"00000000";
41
42 begin
43     process (CLK, temp, Pc_In)
44     begin
45         Pc_Out<= temp;
46         if FALLING_EDGE (CLK) THEN temp <= Pc_In;
47         END IF;
48     end process;
49
50
51 end Behavioral;
```

2) Instruction Memory

VHDL Module :

```
33 entity InstMem is
34     Port ( Address : in  STD_LOGIC_VECTOR (31 downto 0);
35           Instruction : out STD_LOGIC_VECTOR (31 downto 0);
36           CLK : in STD_LOGIC);
37 end InstMem;
38
39 architecture Behavioral of InstMem is
40     type INSTArray is array (0 to 31) of STD_LOGIC_VECTOR (7 downto 0);
41     signal IM : INSTArray:= (
42         x"00",x"85",x"10",x"20",    --add $v0, $a0, $a1
43         x"AC",x"02",x"00",x"08",    --sw $v0, 8($zero)
44         x"8C",x"06",x"00",x"08",    --lw $a2, 8($zero)
45         x"10",x"46",x"00",x"01",    --beq $v0, $a2, Good_Processor
46         x"00",x"46",x"88",x"2A",    --slt $s1, $v0, $a2
47         x"00",x"A4",x"88",x"22",    --Good_Processor: sub $s1, $a1, $a0
48         x"00",x"00",x"00",x"00",
49         x"00",x"00",x"00",x"00");
50
51 begin
52
53     Instruction(31 downto 24) <= IM(to_integer(unsigned(Address)));
54     Instruction(23 downto 16) <= IM(to_integer(unsigned(Address))+1);
55     Instruction(15 downto 8) <= IM(to_integer(unsigned(Address))+2);
56     Instruction(7 downto 0) <= IM(to_integer(unsigned(Address))+3);
57
58 end Behavioral;
```

3) Register File

VHDL Module:

```
32 entity RegisterFile is
33     Port ( ReadReg1 : in  STD_LOGIC_VECTOR (4 downto 0);
34           ReadReg2 : in  STD_LOGIC_VECTOR (4 downto 0);
35           WriteReg  : in  STD_LOGIC_VECTOR (4 downto 0);
36           WriteData : in  STD_LOGIC_VECTOR (31 downto 0);
37           RegWrite  : in  STD_LOGIC;
38           ReadData1 : out STD_LOGIC_VECTOR (31 downto 0);
39           ReadData2 : out STD_LOGIC_VECTOR (31 downto 0);
40           CLK       : in  STD_LOGIC);
41
42 end RegisterFile;

44 architecture Behavioral of RegisterFile is
45     type RegtypeFile is array (0 to 31) of STD_LOGIC_VECTOR (31 downto 0);
46     signal RegArray : RegtypeFile:= (X"00000000",X"00000000",
47                                     X"00000000",X"00000000",
48                                     X"00000005",X"00000007",
49                                     X"00000000",X"00000000",|
50                                     X"00000000",X"00000000",
51                                     X"00000000",X"00000000",
52                                     X"00000000",X"00000000",
53                                     X"00000000",X"00000000",
54                                     X"00000000",X"00000000",
55                                     X"00000000",X"00000000",
56                                     X"00000000",X"00000000",
57                                     X"00000000",X"00000000",
58                                     X"00000000",X"00000000",
59                                     X"00000000",X"00000000",
60                                     X"00000000",X"00000000",
61                                     X"00000000",X"00000000");
62     --ThirdLine $a0,$a1
63 begin
64     Process (RegWrite,CLK, ReadReg1,ReadReg2,WriteReg,WriteData,RegWrite)
65     begin
66         ReadData1 <= RegArray(to_integer(unsigned(ReadReg1)));
67         ReadData2 <= RegArray(to_integer(unsigned(ReadReg2)));
68         if (rising_edge(CLK) and RegWrite = '1')
69         then
70             RegArray(to_integer(unsigned(WriteReg)))<= WriteData ;
71         end if;
72     end process;
73 end Behavioral;
```

4) ALU

VHDL Module:

```
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.STD_LOGIC_ARITH.ALL;
23 use IEEE.STD_LOGIC_UNSIGNED.ALL;
24 |
25 entity ALU4Bit is
26     Port ( A : in  STD_LOGIC_VECTOR (31 downto 0);
27           B : in  STD_LOGIC_VECTOR (31 downto 0);
28           ALUin : in  STD_LOGIC_VECTOR (3 downto 0);
29           zero : out  STD_LOGIC;
30           result : out  STD_LOGIC_VECTOR (31 downto 0));
31 end ALU4Bit;
32
33
34
35 begin
36 process(A,B,ALUin)
37 begin
38     if ALUin = "0000"
39         then result <= A and B ;
40     elsif ALUin = "0001"
41         then result <= A or B;
42     elsif ALUin = "0111"
43         then if A < B then result <= X"00000001";
44             else result <= X"00000000";
45         end if;
46     elsif ALUin = "0010"
47         then result <= A + B;
48     elsif ALUin = "0110"
49         then result <= A - B;
50     elsif ALUin = "1100"
51         then result <= A nor B;
52     end if ;
53     if A = B
54     then zero <= '1';
55     else zero <= '0';
56     end if ;
57 end PROCESS;
58
59 end Behavioral;
```


5) ALU Control

VHDL Module:

```
32 entity ALU_Control is
33   Port ( ALUOP : in  STD_LOGIC_VECTOR (1 downto 0);
34         FuncField : in  STD_LOGIC_VECTOR (5 downto 0);
35         Operation : out  STD_LOGIC_VECTOR (3 downto 0));
36 end ALU_Control;
37
38 architecture Behavioral of ALU_Control is
39
40 begin
41 process(ALUOP,FuncField)
42 begin
43 if (ALUOP = "00") then Operation <= "0010";
44 elsif (ALUOP = "01") then Operation <= "0110";
45 elsif ((ALUOP = "10") and ((FuncField(3)='0')and(FuncField(2)='0') and (FuncField(1)='0')and (FuncField(0)='0')))) then Operation <= "0010";
46 elsif ((ALUOP = "10") and ((FuncField(3)='0')and(FuncField(2)='1') and (FuncField(1)='0')and (FuncField(0)='0')))) then Operation <= "0000";
47 elsif ((ALUOP = "10") and ((FuncField(3)='0')and(FuncField(2)='1') and (FuncField(1)='0')and (FuncField(0)='1')))) then Operation <= "0001";
48 elsif ((ALUOP(1) = '1') and ((FuncField(3)='0')and(FuncField(2)='0') and (FuncField(1)='1')and (FuncField(0)='0')))) then Operation <= "0110";
49 elsif ((ALUOP(1) = '1') and ((FuncField(3)='1')and(FuncField(2)='0') and (FuncField(1)='1')and (FuncField(0)='0')))) then Operation <= "0111";
50 end if ;
51 end process;
52 end Behavioral;
```

6) Control Unit

VHDL Module:

```
33 entity Control is
34   Port ( OP : in  STD_LOGIC_VECTOR (5 downto 0);
35         RegDst : out  STD_LOGIC;
36         ALUSrc : out  STD_LOGIC;
37         MemtoReg : out  STD_LOGIC;
38         RegWrite : out  STD_LOGIC;
39         MemRead : out  STD_LOGIC;
40         MemWrite : out  STD_LOGIC;
41         Branch : out  STD_LOGIC;
42         ALUOP0 : out  STD_LOGIC;
43         ALUOP1 : out  STD_LOGIC);
44 end Control;
45
46 architecture Behavioral of Control is
47
48 begin
49 PROCESS(OP)
50 BEGIN
51 IF OP = "000000" THEN RegDst <= '1'; ALUSrc <= '0';MemtoReg <= '0';RegWrite <='1';MemRead <= '0';MemWrite <= '0';Branch <= '0';ALUOP0 <= '1';ALUOP1 <= '0';
52 ELSIF OP = "100011" THEN RegDst <= '0'; ALUSrc <= '1';MemtoReg <= '1';RegWrite <='1';MemRead <= '1';MemWrite <= '0';Branch <= '0';ALUOP0 <= '0';ALUOP1 <= '0';
53 ELSIF OP = "101011" THEN ALUSrc <= '1';RegWrite <='0';MemRead <= '0';MemWrite <= '1';Branch <= '0';ALUOP0 <= '0';ALUOP1 <= '0';
54 ELSIF OP = "000100" THEN ALUSrc <= '0';RegWrite <='0';MemRead <= '0';MemWrite <= '0';Branch <= '1';ALUOP0 <= '0';ALUOP1 <= '1';
55
56 END IF;
57 END PROCESS;
```

7) Memory Unit

VHDL Module:

```
32 entity MemoryUnit is
33     Port ( MemRead : in  STD_LOGIC;
34           MemWrite : in  STD_LOGIC;
35           Address  : in  STD_LOGIC_VECTOR (31 downto 0);
36           DataWrite : in  STD_LOGIC_VECTOR (31 downto 0);
37           DataRead  : out STD_LOGIC_VECTOR (31 downto 0);
38           CLK       : in  STD_LOGIC);
39 end MemoryUnit;
40
41 architecture Behavioral of MemoryUnit is
42     type MEMArray is array (0 to 35) of STD_LOGIC_VECTOR (7 downto 0);
43     signal RAM: MEMArray:= (x"AB",x"CD",x"EF",x"00",
44                             x"75",x"74",x"65",x"72",
45                             x"20",x"41",x"72",x"63",
46                             x"68",x"69",x"74",x"65",
47                             x"12",x"34",x"56",x"78",
48                             x"7F",x"7F",x"6D",x"6D",
49                             x"00",x"00",x"00",x"00",
50                             x"78",x"78",x"6A",x"6A",
51                             x"00",x"00",x"00",x"01");
52
53 begin
54     process (MemRead,MemWrite,Address,CLK)
55     begin
56         if (MemRead = '1' and MemWrite = '0')
57         then DataRead(31 downto 24) <= RAM(to_integer(unsigned(Address)));
58          DataRead(23 downto 16) <= RAM(to_integer(unsigned(Address)+1));
59          DataRead(15 downto 8) <= RAM(to_integer(unsigned(Address)+2));
60          DataRead(7 downto 0) <= RAM(to_integer(unsigned(Address)+3));
61         elsif (MemRead = '0' and MemWrite = '1' and rising_edge(CLK))
62         then RAM(to_integer(unsigned(Address))) <= DataWrite(31 downto 24);
63          RAM(to_integer(unsigned(Address)+1)) <= DataWrite(23 downto 16);
64          RAM(to_integer(unsigned(Address)+2)) <= DataWrite(15 downto 8);
65          RAM(to_integer(unsigned(Address)+3)) <= DataWrite(7 downto 0);
66         end if ;
67     end process;
68 end Behavioral;
```

8) Adders

ADDER for 32 bit inputs

VHDL Module:

```
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.STD_LOGIC_ARITH.ALL;
23 use IEEE.STD_LOGIC_UNSIGNED.ALL;
24 |
25
26 entity Adder32Bit is
27     Port ( In1 : in  STD_LOGIC_VECTOR (31 downto 0);
28           In2 : in  STD_LOGIC_VECTOR (31 downto 0);
29           Sum : out  STD_LOGIC_VECTOR (31 downto 0));
30 end Adder32Bit;
31
32 architecture Behavioral of Adder32Bit is
33
34 begin
35 process(In1, In2)
36 begin
37 Sum <= In1 + In2;
38 end process;
39
40 end Behavioral;
```

ADDER for PC+4

VHDL Module:

```
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 USE IEEE.STD_LOGIC_ARITH.ALL;
23 USE IEEE.STD_LOGIC_UNSIGNED.ALL;
24
25 |
26
27 entity Adder4Bit is
28     Port ( INPUT1 : in  STD_LOGIC_VECTOR (31 downto 0);
29           OUTPUT1 : out  STD_LOGIC_VECTOR (31 downto 0));
30 end Adder4Bit;
31
32 architecture Behavioral of Adder4Bit is
33
34 begin
35 process(INPUT1)
36 begin
37 OUTPUT1 <= INPUT1 + X"00000004";
38 end process;
39
40 end Behavioral;
```


9) Muxes

2-1 32Bit Mux

VHDL Module:

```
32 entity Mux2_1 is
33     Port ( IN1 : in  STD_LOGIC_VECTOR (31 downto 0);
34           IN2 : in  STD_LOGIC_VECTOR (31 downto 0);
35           S : in  STD_LOGIC;
36           OUTMUX : out  STD_LOGIC_VECTOR (31 downto 0));
37 end Mux2_1;
38
39 architecture Behavioral of Mux2_1 is
40 begin
41     process (IN1,IN2,S)
42     begin
43         if (S = '0') then OUTMUX <= IN1;
44         elsif (S = '1') then OUTMUX <= IN2;
45         end if ;
46     end process;
47
48 end Behavioral;
```

2-1 5Bit Mux

VHDL Module:

```
32 entity MUX_5 is
33     Port ( A : in  STD_LOGIC_VECTOR (4 downto 0);
34           B : in  STD_LOGIC_VECTOR (4 downto 0);
35           OUTM : out  STD_LOGIC_VECTOR (4 downto 0);
36           S : in  STD_LOGIC);
37 end MUX_5;
38
39 architecture Behavioral of MUX_5 is
40
41 begin
42     process (A,B,S)
43     begin
44         if (S = '0') then OUTM <= A;
45         elsif (S = '1') then OUTM <= B;
46         end if ;
47     end process;
48
49
50 end Behavioral;
```

10) Shift Left

VHDL Module:

```
32 entity ShiftLeft is
33     Port ( Inshift : in  STD_LOGIC_VECTOR (31 downto 0);
34           Outshift : out  STD_LOGIC_VECTOR (31 downto 0));
35 end ShiftLeft;
36
37 architecture Behavioral of ShiftLeft is
38
39 begin
40
41 process(Inshift)
42 begin
43 Outshift(1 downto 0) <= "00";
44 Outshift(31 downto 2) <= Inshift(29 downto 0);
45 end process;
46
47 end Behavioral;
```

11) Sign Extend

VHDL Module:

```
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.STD_LOGIC_ARITH.ALL;
23 use IEEE.STD_LOGIC_UNSIGNED.ALL;|
24 entity SignExtend32Bit is
25     Port ( A : in  STD_LOGIC_VECTOR (15 downto 0);
26           B : out  STD_LOGIC_VECTOR (31 downto 0));
27 end SignExtend32Bit;
28
29 architecture Behavioral of SignExtend32Bit is
30
31 begin
32 process (A)
33 begin
34 if (A(15)='0') then B <= X"00000000" + A;
35 elsif (A(15)='1') then B <= X"ffff0000" + A;
36 end if;
37 end process;
38
39 end Behavioral;
```

The Main Program Port Mapping and Components

```
32 entity PROJECT_MIPS is
33     Port ( CLK1 : in  STD_LOGIC);
34 end PROJECT_MIPS;
35
36 architecture Behavioral of PROJECT_MIPS is
37     --COMPONENTS
38
39     COMPONENT Adder32Bit is
40         Port ( In1 : in  STD_LOGIC_VECTOR (31 downto 0);
41               In2 : in  STD_LOGIC_VECTOR (31 downto 0);
42               Sum : out STD_LOGIC_VECTOR (31 downto 0));
43     end component ;
44     COMPONENT MUX_5 is
45         Port ( A : in  STD_LOGIC_VECTOR (4 downto 0);
46               B : in  STD_LOGIC_VECTOR (4 downto 0);
47               OUTM : out STD_LOGIC_VECTOR (4 downto 0);
48               S : in  STD_LOGIC);
49     end COMPONENT MUX_5;
50     component Adder4Bit is
51         Port ( INPUT1 : in  STD_LOGIC_VECTOR (31 downto 0);
52               OUTPUT1 : out STD_LOGIC_VECTOR (31 downto 0));
53     end component;
54     component ALU4Bit is
55         Port ( A : in  STD_LOGIC_VECTOR (31 downto 0);
56               B : in  STD_LOGIC_VECTOR (31 downto 0);
57               ALUin : in  STD_LOGIC_VECTOR (3 downto 0);
58               zero : out STD_LOGIC;
59               result : out STD_LOGIC_VECTOR (31 downto 0));
60     end component;
61     component ALU_Control is
62         Port ( ALUOP : in  STD_LOGIC_VECTOR (1 downto 0);
63               FuncField : in  STD_LOGIC_VECTOR (5 downto 0);
64               Operation : out STD_LOGIC_VECTOR (3 downto 0));
65     end component ;
66     component Control is
67         Port ( OP : in  STD_LOGIC_VECTOR (5 downto 0);
68               RegDst : out STD_LOGIC;
69               ALUSrc : out STD_LOGIC;
70               MemtoReg : out STD_LOGIC;
71               RegWrite : out STD_LOGIC;
72               MemRead : out STD_LOGIC;
73               MemWrite : out STD_LOGIC;
74               Branch : out STD_LOGIC;
75               ALUOP0 : out STD_LOGIC;
76               ALUOP1 : out STD_LOGIC);
77     end component ;
78     component InstMem is
79         Port ( Address : in  STD_LOGIC_VECTOR (31 downto 0);
80               Instruction : out STD_LOGIC_VECTOR (31 downto 0);
81               CLK : in  STD_LOGIC);
82     end component ;
83     component MemoryUnit is
84         Port ( MemRead : in  STD_LOGIC;
85               MemWrite : in  STD_LOGIC;
86               Address : in  STD_LOGIC_VECTOR (31 downto 0);
87               DataWrite : in  STD_LOGIC_VECTOR (31 downto 0);
88               DataRead : out STD_LOGIC_VECTOR (31 downto 0);
89               CLK : in  STD_LOGIC);
90     end component;
91     component Mux2_1 is
92         Port ( IN1 : in  STD_LOGIC_VECTOR (31 downto 0);
93               IN2 : in  STD_LOGIC_VECTOR (31 downto 0);
94               S : in  STD_LOGIC;
95               OUTMUX : out STD_LOGIC_VECTOR (31 downto 0));
96     end component;
```

```

97 component PCounter is
98     Port ( Pc_In : in  STD_LOGIC_VECTOR (31 downto 0);
99           CLK : in  STD_LOGIC;
100           Pc_Out : out STD_LOGIC_VECTOR (31 downto 0));
101 end component;
102 component RegisterFile is
103     Port ( ReadReg1 : in  STD_LOGIC_VECTOR (4 downto 0);
104           ReadReg2 : in  STD_LOGIC_VECTOR (4 downto 0);
105           WriteReg : in  STD_LOGIC_VECTOR (4 downto 0);
106           WriteData : in  STD_LOGIC_VECTOR (31 downto 0);
107           RegWrite : in  STD_LOGIC;
108           ReadData1 : out STD_LOGIC_VECTOR (31 downto 0);
109           ReadData2 : out STD_LOGIC_VECTOR (31 downto 0);
110           CLK : in  STD_LOGIC);
111 end component;
112 component ShiftLeft is
113     Port ( Inshift : in  STD_LOGIC_VECTOR (31 downto 0);
114           Outshift : out STD_LOGIC_VECTOR (31 downto 0));
115 end component;
116 component SignExtend32Bit is
117     Port ( A : in  STD_LOGIC_VECTOR (15 downto 0);
118           B : out STD_LOGIC_VECTOR (31 downto 0));
119 end component ;
120 --SIGNALS
121 --PC Signals
122 SIGNAL PC_OUT : STD_LOGIC_VECTOR (31 DOWNTO 0);
123 SIGNAL PC_ADDER_OUT : STD_LOGIC_VECTOR (31 DOWNTO 0);
124 SIGNAL PC_NEW_ADDRESS : STD_LOGIC_VECTOR (31 DOWNTO 0);
125 --Instructions
126 SIGNAL INSTRUCTION1: STD_LOGIC_VECTOR (31 DOWNTO 0);
127 SIGNAL OPCODE_CU : STD_LOGIC_VECTOR (5 DOWNTO 0);
128 SIGNAL RS : STD_LOGIC_VECTOR (4 DOWNTO 0);
129 SIGNAL RT : STD_LOGIC_VECTOR (4 DOWNTO 0);
130 SIGNAL RD : STD_LOGIC_VECTOR (4 DOWNTO 0);
131 SIGNAL FUNCTION_FIELD : STD_LOGIC_VECTOR (5 DOWNTO 0);
132 SIGNAL INST15_0 : STD_LOGIC_VECTOR (15 DOWNTO 0);
133 SIGNAL REGISTER_MUX : STD_LOGIC_VECTOR (4 DOWNTO 0);
134 -- Register outputs
135 SIGNAL R1 : STD_LOGIC_VECTOR (31 DOWNTO 0);
136 SIGNAL R2 : STD_LOGIC_VECTOR (31 DOWNTO 0);
137 -- ALU IN and OUT
138 SIGNAL IMMEDIATE : STD_LOGIC_VECTOR (31 DOWNTO 0);
139 SIGNAL SHIFTLLEFT_OUT : STD_LOGIC_VECTOR (31 DOWNTO 0);
140 SIGNAL R2_IMMEDIATE_MUX : STD_LOGIC_VECTOR (31 DOWNTO 0);
141 SIGNAL ALUCONTROL_OUT : STD_LOGIC_VECTOR (3 DOWNTO 0);
142 SIGNAL ALU_RES_OUT : STD_LOGIC_VECTOR (31 DOWNTO 0);
143 SIGNAL ZERO_CU : STD_LOGIC;
144 --Branch
145 SIGNAL NEW_BRANCH : STD_LOGIC_VECTOR (31 DOWNTO 0);
146 SIGNAL BRANCH_CONTROLLER : STD_LOGIC;
147 --Memory
148 SIGNAL MEM_READ_OUT : STD_LOGIC_VECTOR (31 DOWNTO 0);
149 SIGNAL WRITE_REG : STD_LOGIC_VECTOR (31 DOWNTO 0);
150 --Control Unit
151 SIGNAL REGDST_CU : STD_LOGIC;
152 SIGNAL BRANCH_CU : STD_LOGIC;
153 SIGNAL MEMREAD_CU : STD_LOGIC;
154 SIGNAL MEMTOREG_CU : STD_LOGIC;
155 SIGNAL MEMWRITE_CU : STD_LOGIC;
156 SIGNAL ALUSRC_CU : STD_LOGIC;
157 SIGNAL REGWRITE_CU : STD_LOGIC;
158 SIGNAL ALUOP_CU : STD_LOGIC_VECTOR (1 DOWNTO 0);
159

```

Port Mapping:

```
160 begin
161
162 --BREAKING DOWN INSTRUCTION(31 - 0)
163 OPCODE_CU <= INSTRUCTION1(31 DOWNT0 26);
164 RS <= INSTRUCTION1(25 DOWNT0 21);
165 RT <= INSTRUCTION1(20 DOWNT0 16);
166 RD <= INSTRUCTION1(15 DOWNT0 11);
167 INST15_0 <= INSTRUCTION1(15 DOWNT0 0);
168 FUNCTION_FIELD <= INSTRUCTION1(5 DOWNT0 0);
169 -- BRANCH_CONTROLLER
170 BRANCH_CONTROLLER <= (BRANCH_CU AND ZERO_CU);
171 --CALCULATING NEW ADDRESS OF BRANCH
172 PC_BRANCH_ADDRESS : Adder32Bit
173   Port MAP( In1 => PC_ADDER_OUT,
174             In2 => SHIFTLLEFT_OUT,
175             Sum => NEW_BRANCH);
176 --CALCULATING PC + 4
177 PC_NEXT_INSTRUCTION : Adder4Bit
178   Port MAP( INPUT1 => PC_OUT ,
179             OUTPUT1 => PC_ADDER_OUT );
180 --SELECTING THE NEW BRANCH OR PC+4
181 BRANCH_MUX : Mux2_1
182   Port MAP( IN1 => PC_ADDER_OUT,
183             IN2 => NEW_BRANCH,
184             S => BRANCH_CONTROLLER,
185             OUTMUX => PC_NEW_ADDRESS );
186
187 --FETCHING INSTRUCTION
188 INST_MEM : InstMem
189   Port MAP( Address => PC_OUT ,
190             Instruction => INSTRUCTION1,
191             CLK => CLK1);
192
193 --GETTING IMMEDIATE VALUE
194 SIGN_EXTEND : SignExtend32Bit
195   Port MAP( A => INST15_0 ,
196             B => IMMEDIATE);
197 --SELECTING FOR WRITE REG
198 MUX_REGISTER : MUX_5
199   Port MAP ( A => RT ,
200             B => RD ,
201             OUTM => REGISTER_MUX,
202             S => REGDST_CU);
203 --GETTING REGISTERS
204 REGISTER_FILE : RegisterFile
205   Port MAP( ReadReg1 => RS,
206             ReadReg2 => RT,
207             WriteReg => REGISTER_MUX,
208             WriteData => WRITE_REG,
209             ReadData1 => R1,
210             ReadData2 => R2,
211             RegWrite => REGWRITE_CU,
212             CLK => CLK1);
213 --GETTING OPERATIONS
214 ALUCONTROL : ALU_Control
215   Port MAP( ALUOP => ALUOP_CU ,
216             FuncField => FUNCTION_FIELD ,
217             Operation => ALUCONTROL_OUT );
218 --SELECTING R2 OR IMMEDIATE VALUE
219 ALU_MUX1 : Mux2_1
220   Port MAP( IN1 => R2,
221             IN2 => IMMEDIATE,
222             S => ALUSRC_CU,
223             OUTMUX => R2_IMMEDIATE_MUX );
```



```

224 ALU : ALU4Bit
225     Port MAP( A => R1,
226               B => R2_IMMEDIATE_MUX,
227               ALUin => ALUCONTROL_OUT ,
228               zero => ZERO_CU,
229               result => ALU_RES_OUT );
230 MEM : MemoryUnit
231     Port MAP(
232         MemRead => MEMREAD_CU,
233         MemWrite => MEMWRITE_CU,
234         Address => ALU_RES_OUT,
235         DataWrite => R2,
236         DataRead => MEM_READ_OUT,
237         CLK => CLK1);
238
239 --SELECTING THE DATA TO BE WRITTEN IN THE REGISTER
240 MEM_MUX : Mux2_1
241     Port MAP( IN1 => ALU_RES_OUT,
242               IN2 => MEM_READ_OUT,
243               S => MEMTOREG_CU,
244               OUTMUX => WRITE_REG);
245 --SETTING CONTROL UNIT SIGNALS
246 CONTROL_UNIT : Control
247     Port MAP( OP => OPCODE_CU ,
248               RegDst => REGDST_CU,
249               ALUSrc => ALUSRC_CU,
250               MemtoReg => MEMTOREG_CU,
251               RegWrite => REGWRITE_CU,
252               MemRead => MEMREAD_CU,
253               MemWrite => MEMWRITE_CU,
254               Branch => BRANCH_CU,
255               ALUOP0 => ALUOP_CU(1),
256               ALUOP1 => ALUOP_CU(0));
257
258 SHIFT_LEFT : ShiftLeft
259     Port MAP( Inshift => IMMEDIATE ,
260               Outshift => SHIFTLLEFT_OUT );
261
262
263 PC_COUNT : PCCounter
264     Port MAP( Pc_In => PC_NEW_ADDRESS,
265               CLK => CLK1,
266               Pc_Out => PC_OUT );
267
268 end Behavioral;


```

Simulation of the Design:

1- add \$v0, \$a0, \$a1


This is R-Type Instruction so the operation is the addition of the values in registers \$a0(4) and \$a1(5) and save the result in \$v0(2)

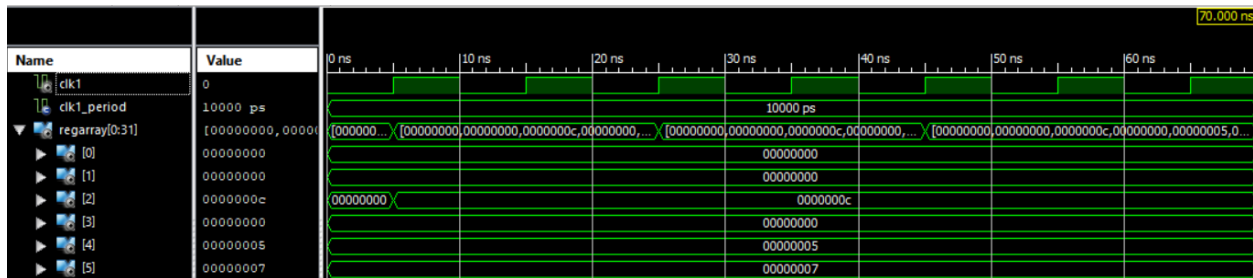5+7 = x(c) as the simulation shows the operation is made correctly.




2- sw \$v0, 8(\$zero)

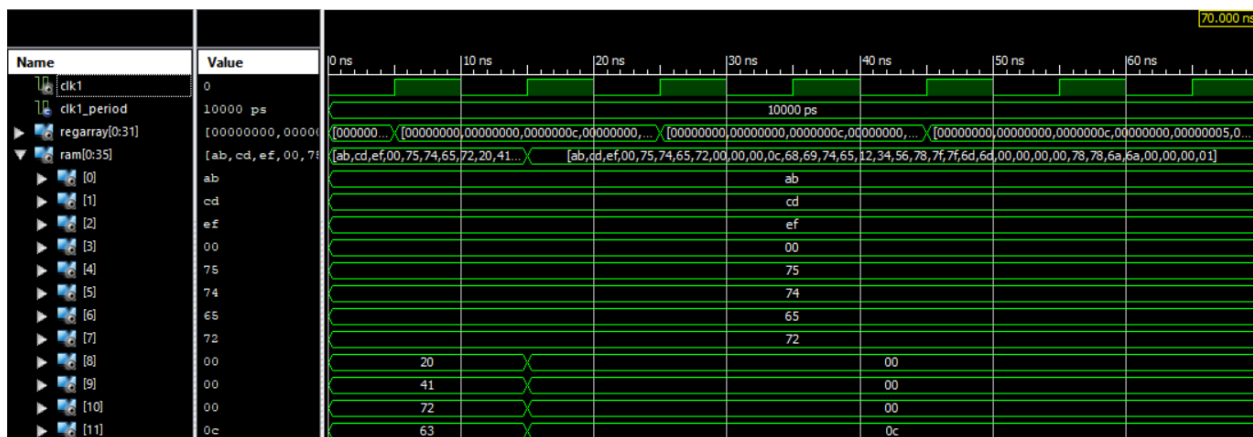This I-Type Instruction were the operation is done by calculating the address to which we will save the data of Register \$v0 in the memory by the addition of the offset *4 with the reference address which is \$zero (As we know from the previous instruction the value in \$v0 is x"0000000c" from 8to 11)



3- lw \$a2, 8(\$zero)

 
This I-Type Instruction were the operation is done by reading the value stored in the memory at Address $8 \times 4 + \$zero$ and save it in the register \$a2(6)



4- beq \$v0, \$a2, Good_Processor

This I-Type Instruction were the operation is done by subtracting the values stored in \$v0("0000000c") and \$a2("0000000c") if the result is zero then a new address is calculated by the addition of the immediate value which is sign extended and shifted to the left by 2 bits with the PC+4 signal calculated

 (after the 4 clock the address after c is 10 but Because the condition was true the address changed to 14 which is the place where our label refers)



5- slt \$s1, \$

| Name | Value | 0 ns | 10 ns | 20 ns | 30 ns | 40 ns | 50 ns | 60 ns | |
|----------------|--|----------|-------|-------|-------|-------|-------|-------|--|
| clk1 | 0 | | | | | | | | |
| clk1_period | 10000 ps | 10000 ps | | | | | | | |
| regarray[0:31] | {00000000, 00000000} | | | | | | | | |

Third Part: the individual's role

7-5 = x(2) as the simulation shows the operation is made correctly

| Name | Value | 0 ns | 10 ns | 20 ns | 30 ns | 40 ns | 50 ns | 60 ns | 70.000 ns |
|----------------|--|--|-------|-------|-------|-------|-------|-------|-----------|
| clk1 | 0 | | | | | | | | |
| clk1_period | 10000 ps | 10000 ps | | | | | | | |
| regarray[0:31] | [00000000, 00000000] | [00000000, 00000000] | | | | | | | |
| [0] | 00000000 | 00000000 | | | | | | | |
| [1] | 00000000 | 00000000 | | | | | | | |
| [2] | 0000000c | 0000000c | | | | | | | |
| [3] | 00000000 | 00000000 | | | | | | | |
| [4] | 00000005 | 00000005 | | | | | | | |
| [5] | 00000007 | 00000007 | | | | | | | |
| [6] | 0000000c | 0000000c | | | | | | | |
| [7] | 00000000 | 00000000 | | | | | | | |
| [8] | 00000000 | 00000000 | | | | | | | |
| [9] | 00000000 | 00000000 | | | | | | | |
| [10] | 00000000 | 00000000 | | | | | | | |
| [11] | 00000000 | 00000000 | | | | | | | |
| [12] | 00000000 | 00000000 | | | | | | | |
| [13] | 00000000 | 00000000 | | | | | | | |
| [14] | 00000000 | 00000000 | | | | | | | |
| [15] | 00000000 | 00000000 | | | | | | | |
| [16] | 00000000 | 00000000 | | | | | | | |
| [17] | 00000002 | 00000002 | | | | | | | |